

CPE 462

VHDL: Simulation and Synthesis

Topic #02 - a) Review of Combinational Logic


Some information on the following slides was taken from:
<http://hyperphysics.phy-astr.gsu.edu>

Basic Gates




1) These are the basic gates we will be dealing with:

- AND, NAND
- BUF, NOT
- OR, NOR
- XOR, XNOR

 
2) While you should know how each logic gate is implemented at the transistor level, in this course we are mainly working at the register-transfer level (RTL).



AND, OR, NOT and BUF

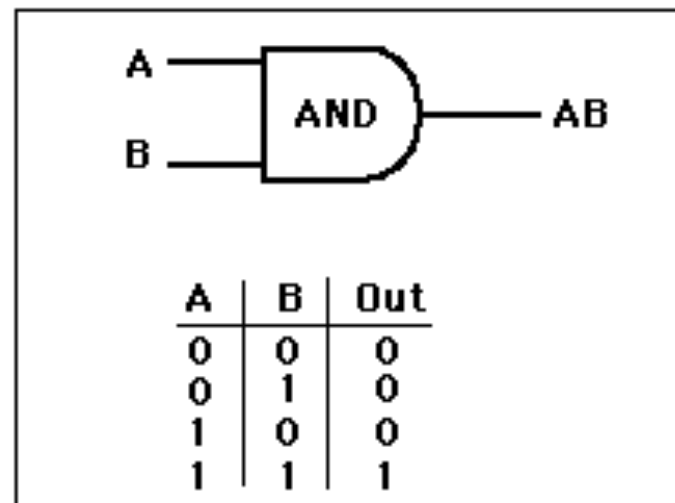
 
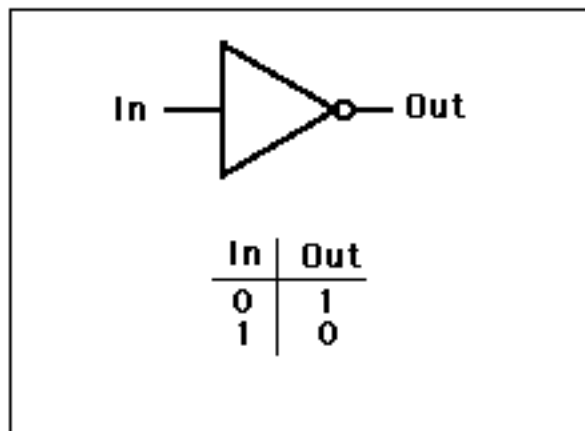


 The AND operation will be signified by AB or $A \cdot B$. Other common mathematical notations for it are $A \wedge B$ and $A \cap B$, called the intersection of A and B.




The OR operation will be signified by $A + B$. Other common mathematical notations for it are $A \vee B$ and $A \cup B$, called the union of A and B.

K'nex implementations of logic gates

 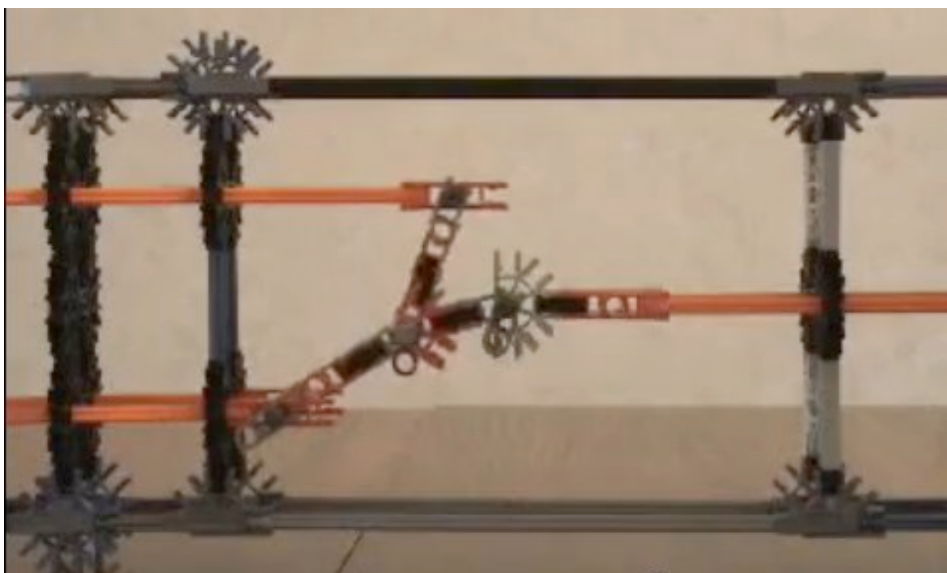 

Water gates


 


AND gate

NAND and NOR


The NAND gate and the NOR gate are universal.

 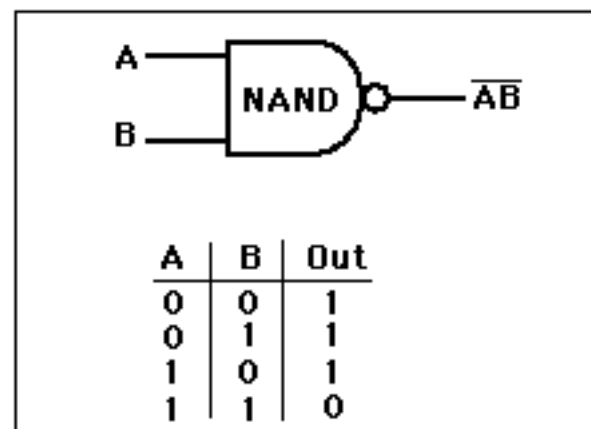This means any combinations of them can be used to accomplish any of the basic logic operations.



NAND gate operations


 
With just NAND gates we can come up with all other basic gates...



A more complex circuit with just NAND gates


Suppose you want a high output when either A or B is high but C is low.

Boolean expression
 $(A + B)\bar{C}$

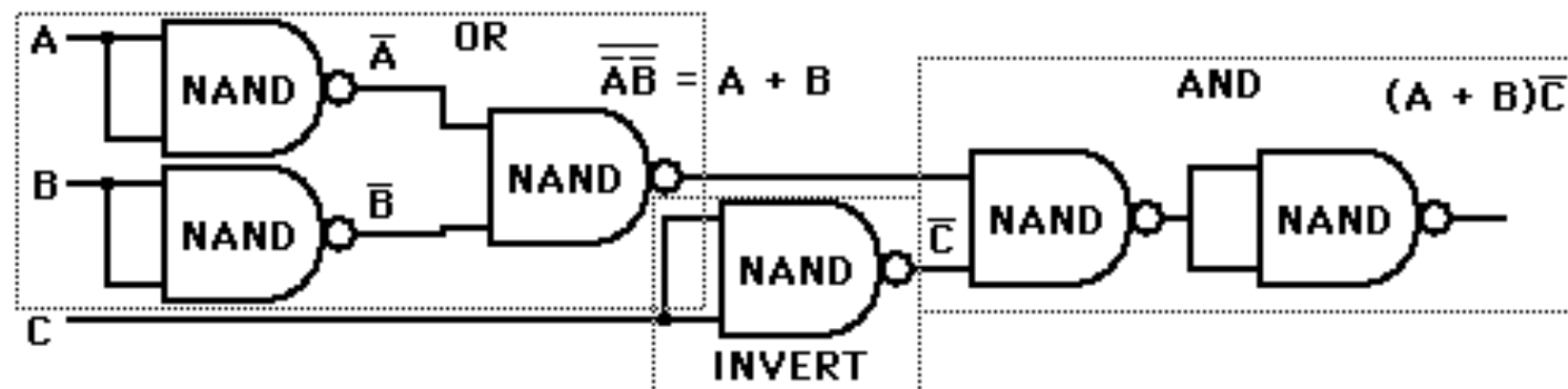 


NOR gate operations

Since NOR gates are also universal...

 


XOR gates

 


The output is high when either of inputs A or B is high, but not if both A and B are high.

Logically, the XOR operation can be seen as either of the following operations:

$$A \oplus B = A\bar{B} + \bar{A}B$$


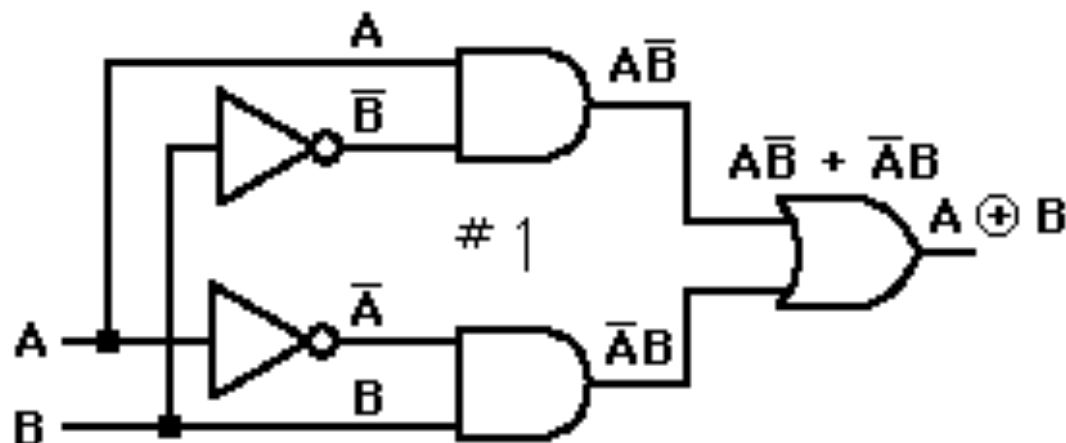


$$A \oplus B = (A + B)(\overline{AB})$$

 


XOR gate implementations

  Implementing XOR gates with NOR and NAND universal gates...



Fluidics

 Fluidics is the use of a fluid to perform analog or digital operations similar to those performed with electronics.



The two gates AND and XOR in one module. The bucket in the center collects the AND output, and the output at the bottom is $A \text{ XOR } B$.

http://www.blikstein.com/paulo/projects/project_water.html

Review of Boolean Logic Rules

NOT Operations (')

$$\begin{aligned}0' &= 1 & A'' &= A \\1' &= 0\end{aligned}$$

AND Operations (.)

$$\begin{aligned}0 \cdot 0 &= 0 & A \cdot 0 &= 0 \\1 \cdot 0 &= 0 & A \cdot 1 &= A \\0 \cdot 1 &= 0 & A \cdot A &= A \\1 \cdot 1 &= 1 & A \cdot A' &= 0\end{aligned}$$

OR Operations (+)

$$\begin{aligned}0 + 0 &= 0 & A + 0 &= A \\1 + 0 &= 1 & A + 1 &= 1 \\0 + 1 &= 1 & A + A &= A \\1 + 1 &= 1 & A + A' &= 1\end{aligned}$$

Associative Law

$$\begin{aligned}(A \cdot B) \cdot C &= A \cdot (B \cdot C) = A \cdot B \cdot C \\(A + B) + C &= A + (B + C) = A + B + C\end{aligned}$$

Distributive Law

$$\begin{aligned}A \cdot (B + C) &= (A \cdot B) + (A \cdot C) \\A + (B \cdot C) &= (A + B) \cdot (A + C)\end{aligned}$$


Commutative Law

$$\begin{aligned}A \cdot B &= B \cdot A \\A + B &= B + A\end{aligned}$$

Precedence

$$\begin{aligned}AB &= A \cdot B \\A \cdot B + C &= (A \cdot B) + C \\A + B \cdot C &= A + (B \cdot C)\end{aligned}$$

What is this circuit output?

 


De'Morgan Rules:

$$\overline{a \cdot b} = \bar{a} + \bar{b}$$

$$\overline{a + b} = \bar{a} \cdot \bar{b}$$

What is this circuit output?

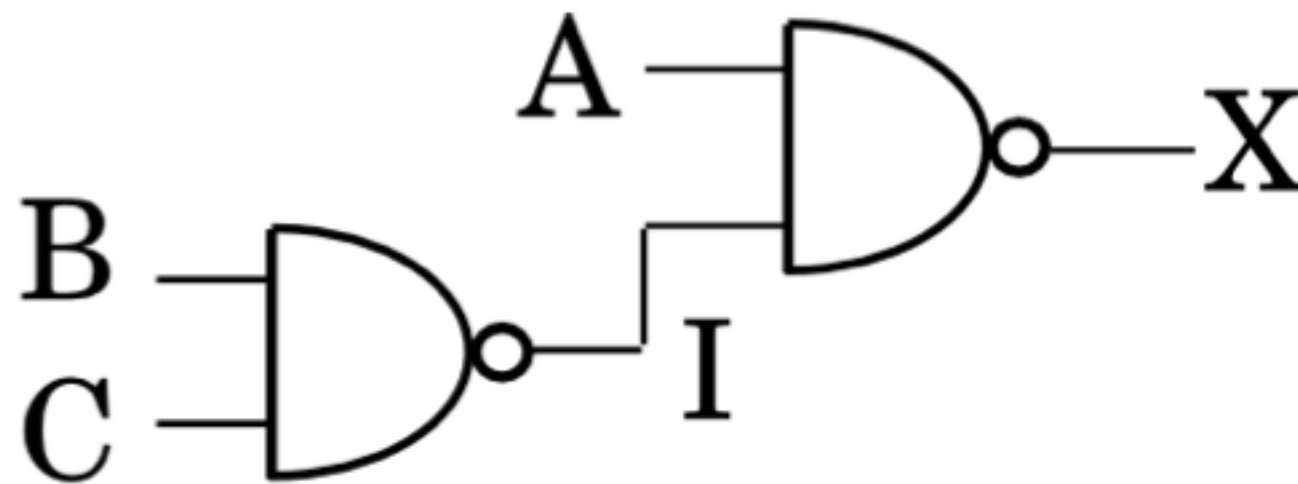

De'Morgan Rules:

$$\overline{a \cdot b} = \bar{a} + \bar{b}$$


$$\overline{a + b} = \bar{a} \cdot \bar{b}$$

$$i = \overline{b \cdot c}$$

$$x = \overline{a \cdot i}$$


$$x = \overline{a \cdot (\overline{b \cdot c})} = \bar{a} + (\overline{\overline{b \cdot c}}) = \bar{a} + (b \cdot c)$$

Alternative is to create a truth table

 


A	B	C	$I = (B \cdot C)'$	$X = (A \cdot I)'$
0	0	0	1	1
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	0	1

 
Graphical Representation of De'Morgan Rules



 Often it is convenient to use just the circle for inversion rather than the whole inverter gate symbol. Doing this we represent de Morgan's theorem graphically as follows:



 And we can now perform the same manipulations that we did using Boolean algebra directly to circuits as we design them:




Apply de Morgan's theorem

Re-group and cancel the inverters

Circuit with just NAND gates



 
Using graphical representations of De'Morgan rules we can convert circuits so they are implemented with just NAND gates.



Circuit with just NAND gates



 Using graphical representations of De'Morgan rules we can convert circuits so they are implemented with just NAND gates.



Review of binary addition: half-adder

$$0 + 0 = 0$$


$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 10$$




INPUTS		OUTPUTS	
A	B	CARRY	SUM
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

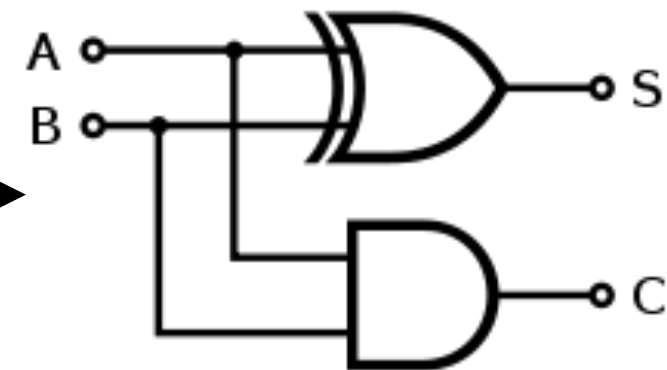


The Carry output is an
AND function, and the Sum
is an XOR.

Review of binary addition: full-adder

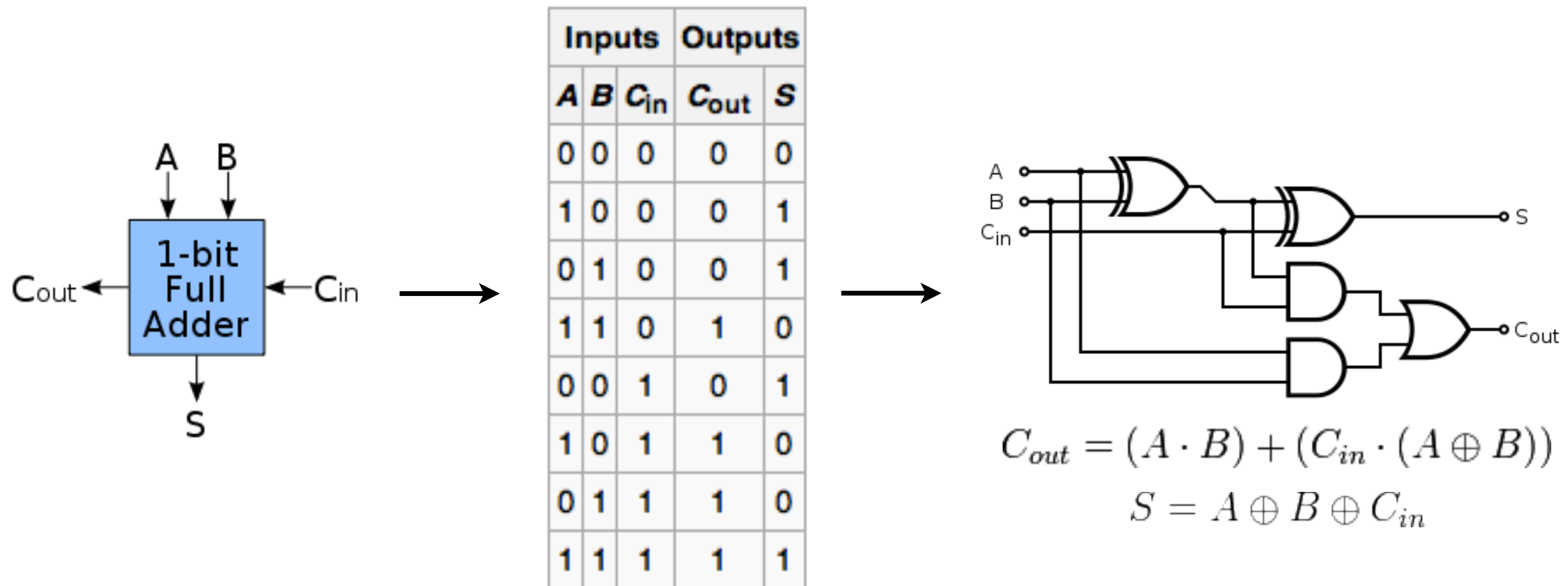


4-Bit adders

4-Bit Adder

 


4-Bit adder with carry lookahead

 


Physical implementation of a 4-Bit adder

 http://knexcomputer.blogspot.com/2006_12_01_archive.html




Multiplexer (MUX)

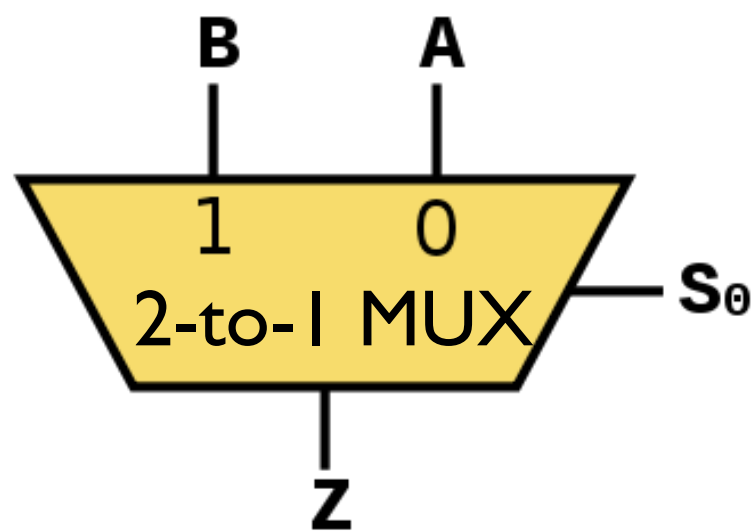


$$Z = (A \cdot \overline{S}) + (B \cdot S)$$

S	A	B	Z
0	1	1	1
	1	0	1
	0	1	0
	0	0	0
1	1	1	1
	1	0	0
	0	1	1
	0	0	0

 
You have n input signals (A and B in this example). With the select bit(s), you determine which input will propagate to the single output.



4-to-1 MUX

 


8-to-1 MUX

 

16-to-1 MUX

4-to-1 MUX

 


$$F = (A \cdot \overline{S_0} \cdot \overline{S_1}) + (B \cdot S_0 \cdot \overline{S_1}) + (C \cdot \overline{S_0} \cdot S_1) + (D \cdot S_0 \cdot S_1)$$

Lets play some MUX games



 
With any number of 2-to-1 MUX gates, implement an AND gate with the function $OUT = A \cdot B$



$OUT = xxx$


Lets play some MUX games

 With any number of 2-to-1 MUX gates, implement an AND gate with the function $OUT = A \cdot B$



$$OUT = a \cdot b + 0 \cdot \bar{b}$$

Single-bit decoder

 

Idea: In the simplest case, you are trying to enable a **single** output, with a combination of input signals.

2 inputs can enable 4 different outputs

...


n inputs can enable 2^n different outputs

Why is this useful? Well, imagine you have an 64 LEDs and you would like to control them individually...

What if I want to turn ON more than one single output?




 For example, how can I set D0 and D3 to HIGH?



What if I want to turn ON more than one single output?

 For example, how can I set D0 and D3 to HIGH?




Use time division multiplexing!

1. Set both A0 and A1 to LOW,
2. Set both A0 and A1 to HIGH
3. Cycle through 1 and 2 very very fast!

If each output was a connected to LED, you wouldn't be able to see the difference!

Slightly more complex decoder

BCD-to-7-segment (multi-output)

 


$$a = A + C + B \bullet D + \bar{B} \bullet \bar{D}$$

$$b = \bar{B} + C \bullet D + \bar{C} \bullet \bar{D}$$


We need to get a boolean logic expression for all outputs... above we find a and b.

	Inputs				Outputs						
	A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	0	0	1	1
	1	0	1	0	x	x	x	x	x	x	x
	1	0	1	1	x	x	x	x	x	x	x
	1	1	0	0	x	x	x	x	x	x	x
	1	1	0	1	x	x	x	x	x	x	x
	1	1	1	0	x	x	x	x	x	x	x
	1	1	1	1	x	x	x	x	x	x	x

 Decoders are so useful that many have been chipped...



IC Decoder
#7448
(\$0.15)

 

Karnaugh map: method to simplify boolean logic expressions

- A Karnaugh Map is a grid-like representation of a truth table
- Here is a sample truth table with 3 inputs(a,b,c) and one output (v)
- $f(a,b,c) = \text{Sum}(3,5,6,7)$
- Draw a diagram with the “strange” order

A	B	C	V
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Diagram illustrating the "strange" order for the Karnaugh map, showing the relationship between variables A, B, and C and the resulting grid layout.

	$\overline{B}\overline{C}$	$\overline{B}C$	BC	$B\overline{C}$
$\overline{A}$	0	1	3	2
A	4	5	7	6

becomes

	$\overline{B}\overline{C}$	$\overline{B}C$	BC	$B\overline{C}$
$\overline{A}$	0	0	1	0
A	0	1	1	1

becomes

	$\overline{B}\overline{C}$	$\overline{B}C$	BC	$B\overline{C}$
$\overline{A}$	0	0	1	0
A	0	1	1	1

$$v = BC + AB + AC$$

Karnaugh map review

$$\text{Out} = \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + \overline{A}B\overline{C} + \overline{A}BC + ABC + AB\overline{C}$$

A \ BC	00	01	11	10
0	1	1	1	1
1			1	1

$$\text{Out} = \overline{A} + B$$

$$\text{Out} = \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + \overline{A}B\overline{C} + \overline{A}BC$$

A \ BC	00	01	11	10
0	1	1	1	1
1				

$$\text{Out} = \overline{A}$$

$$\text{Out} = \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C$$

A \ BC	00	01	11	10
0	1	1		
1				

$$\text{Out} = \overline{A}\overline{B}$$

$$\text{Out} = \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC$$

A \ BC	00	01	11	10
0			1	1
1			1	1

$$\text{Out} = C$$

$$\text{Out} = \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}\overline{C} + ABC$$

A \ BC	00	01	11	10
0	1	1	1	1
1	1			1

$$\text{Out} = \overline{A} + \overline{C}$$

$$\text{Out} = \overline{A}\overline{B}\overline{C} + A\overline{B}\overline{C} + \overline{A}B\overline{C} + AB\overline{C}$$

A \ BC	00	01	11	10
0	1			1
1	1			1

$$\text{Out} = \overline{C}$$

Karnaugh map with 4 variables

Same thing as before... but with more columns and rows.

		$\overline{D} \quad C$ $\overline{C} \quad D$				
		CD	00	01	11	10
$\left[\begin{array}{c} B \\ A \end{array} \right]$	A B	00	0	1	3	2
	01	4	5	7	6	
	11	12	13	15	14	
	10	8	9	11	10	

$$\text{Out} = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}\overline{C}D + \overline{A}\overline{B}C\overline{D} + \overline{A}\overline{B}CD + \overline{A}B\overline{C}\overline{D} + \overline{A}B\overline{C}D + \overline{A}BC\overline{D} + \overline{A}BCD$$

		CD	00	01	11	10
AB	00	1	1	1	1	
	01					
	11					
	10	1	1	1	1	

$$\text{Out} = \overline{B}$$

$$\text{Out} = \overline{A}\overline{B}CD + \overline{A}BCD + ABCD + A\overline{B}CD + AB\overline{C}\overline{D} + AB\overline{C}D + ABC\overline{D}$$

		CD			
		00	01	11	10
AB	00			1	
	01			1	
	11	1	1	1	1
	10			1	

$$\text{Out} = AB + CD$$